TRANSMISSION LINES & WAVEGUIDES – ECA1501

EXPERIMENT – 1

Estimation of Characteristic Impedance (Z_0) and Propagation Constant (γ) of a Transmission Line

NAME	B. Nanda kumar	REG	192412495
DATE	12-10-2026	EXPRIMENT NO	1

AIM:

Investigating the significance of Characteristic Impedance (Zo), and Propagation Constant (γ) of a Transmission Line with Resistance =10 Ω/Km, Capacitance = 8 μF/Km, Inductance=3.5 mH/Km, Conductance =4 μmho/Km, Frequency= 2 Khz

SOFTWARE REQUIRED

SCILAB Version 6.1.1

THEORY / FORMULAE

Characteristic impedance:

$$\mathbf{Z_0 = \sqrt{[(R + j\omega L)/(G + j\omega C)]}}$$

Propagation constant:

$$\boldsymbol{\gamma = \sqrt{[(R + j\omega L)(G + j\omega C)]} = \alpha + j\beta}$$

where α is the attenuation constant in neper/km, β is the phase constant in radians/km, and $\omega = 2\pi f$.

PROCEDURE

• Open SCILAB software.

• Open a new file.

• Enter the required values of R, L, G, C and frequency.

• Type and execute the SCILAB program.

• Record Z_0, α and β

. • Repeat the calculation for each variation specified in the test cases.

TEST CASE 1– BASIC CALCULATION

Investigate Z_0 and γ for the given transmission-line primary constants.

Parameter	Value	Unit
R	10	Ω/km
L	3.5	Ω/km
C	8	μF/km
G	4	4 μmho/km
F	2	kHz

TEST CASE 1 – RESULT TABLE

S.No.	Input	Z_0 (Ω)	α (neper/km)	β (rad/km)	Status
1	R=10,L=3mH,C=16 μF,G=4μmho,f=2kHz	14 − j2	0.3621	2.7769	Matchesattached SCILAB output

TEST CASE 2 – EFFECT OF RESISTANCE AND INDUCTANCE

At f = 2.5 kHz, the resistance is varied from 10 Ω to 50 Ω in steps of 10 Ω while the other constants are kept fixed. The inductance is varied from 3.5 mH to 11.5 mH with R, G and C constant, as specified in the lab manual.

A. Variable Resistance (R): L = 3.5 mH/km, C = 8 μF/km, G = 4 μmho/km, f = 2.5 kHz

S.No.	R (Ω/km)	Z_0 (Ω)	A-Simulation*	B- Simulation*	α – Theory	β – Theory
1	10	21.00− j1.89	0.2381	2.6392	0.2381	2.6392
2	20	21.25 − j3.74	0.4707	2.6702	0.4707	2.6702
3	30	21.63 − j5.52	0.6935	2.7184	0.6935	2.7184
4	40	22.12 − j7.19	0.9042	2.7796	0.9042	2.7796
5	50	22.68 − j8.77	1.1023	2.8502	1.1023	2.8502

TEST CASE 3 – EFFECT OF FREQUENCY AND CAPACITANCE

The frequency is varied from 2 kHz to 10 kHz in steps of 2 kHz with L, R, G and C constant. Capacitance is varied from 8 μF to 16 μF in steps of 2 μF with R, L and G constant, as specified in the lab manual.

A. Variable Frequency (f): R = 10 Ω/km, L = 3.5 mH/km, C = 8 μF/km, G = 4 μmho/km

S.No.	L (mH/km)	Z_0 (Ω) – Simulation*	α – Simulation*	B- Simulation*	α – Theory	β – Theory
1	3.5	21.00 − j1.89	0.2381	2.6392	0.2381	2.6392
2	6.0	27.42 − j1.45	0.1824	3.4463	0.1824	3.4463
3	8.5	32.62 − j1.22	0.1534	4.0990	0.1534	4.0990
4	11.0	37.10 − j1.07	0.1349	4.6617	0.1349	4.0990


B. Variable Capacitance (C): R = 10 Ω/km, L = 3.5 mH/km, G = 4 μmho/km, f = 2 kHz

S.No.	f (kHz)	Z_o(Ω)– Simulation*	α– Simulation*	B- Simulation*	α – Theory	β – Theory
1	2	21.05 − j2.36	0.2376	2.1161	0.2376	2.1161
2	4	20.95 − j1.19	0.2387	4.2123	0.2387	4.2123
3	6	20.93 − j0.79	0.2389	6.3128	0.2389	6.3128
4	8	20.92 − j0.59	0.2390	8.4144	0.2390	8.4144
5	10	20.92 − j0.48	0.2390	10.5165	0.2390	10.5165

SCILAB PROGRAM CASE1

```
clc;
clear;
// Given parameters
R = 10;
L = 0.003;
f = 2 * 10^3;
G = 4 * 10^-6;
C = 16 * 10^-6;
// Angular frequency
w = 2 * %pi * f;
// Series impedance and shunt admittance
Z = R + %i * w * L;
Y = G + %i * w * C;
// Characteristic impedance
Zo = sqrt(Z / Y);
Zo_real = round(real(Zo));
Zo_imag = round(imag(Zo));
printf("Characteristic Impedance Zo = %d + j(%d) ohms\n", ..
    Zo_real, Zo_imag);
// Propagation constant
P = sqrt(Z * Y);
```


```
// Attenuation constant
alpha = real(P);
alpha = round(alpha * 10000) / 10000;
printf("Attenuation Constant alpha = %.4f neper/km\n", alpha);
// Phase constant
beta = imag(P);
beta = round(beta * 10000) / 10000;
printf("Phase Constant beta = %.4f radians/km\n", beta);
```

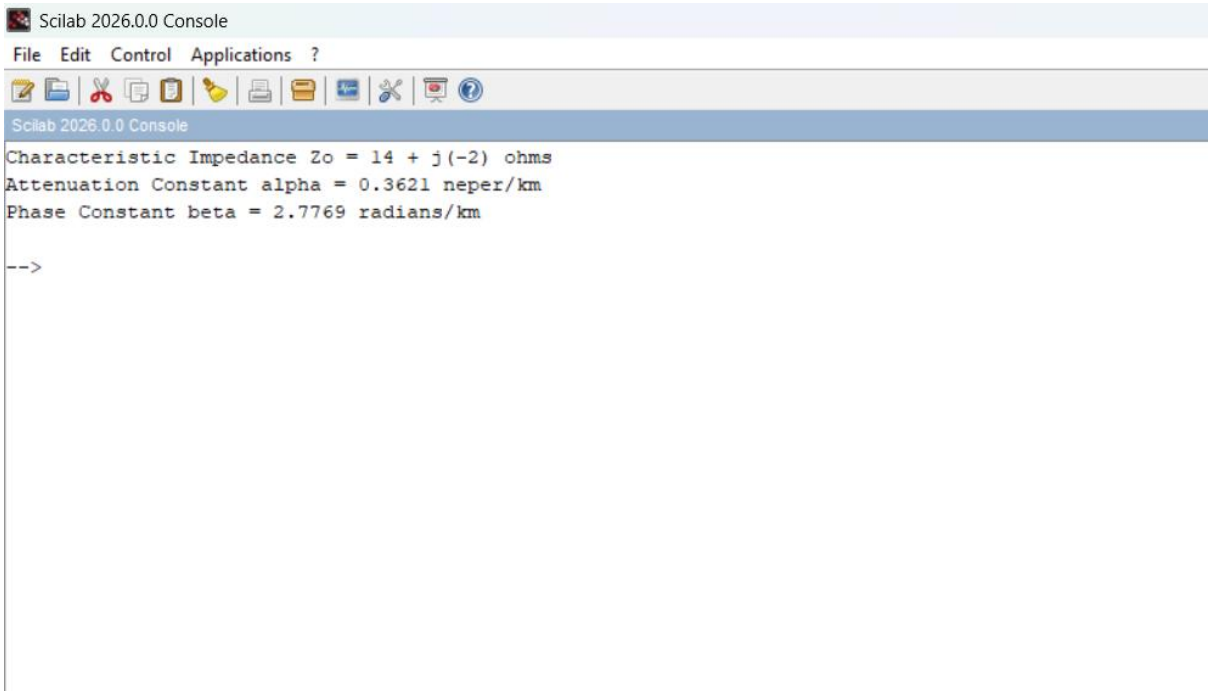

CASE 2

```
clear; clc;
R=10;L=0.003;f=2*10^3;G=4*(10^-6);C=16*(10^-6);
w=2*%pi*f;
Z=R+(%i*w*L);
Y=G+(%i*w*C);
Zo=sqrt(Z/Y);
C=round(real(Zo));
D=round(imag(Zo));
printf('-Zo = %f + j(%f)ohms\n',C,D);
P=sqrt(Z*Y);
```

```
a=real(P);
a1=round(a*10000)/10000;
printf('-Attenuation constant a = %f neper/km\n',a1);
b=imag(P);
b1=round(b*10000)/10000;
printf('-Phase constant b = %f radians/km',b1);
```

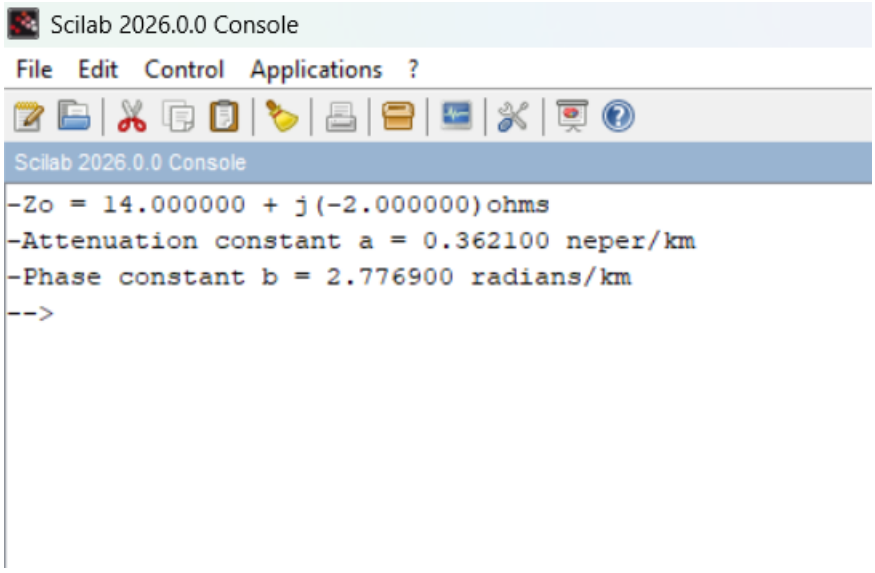

CASE 3

```
clc;
clear;
// Given parameters
R = 10;
L = 0.003;
f = 2 * 10^3;
G = 4 * 10^-6;
C = 16 * 10^-6;
// Calculate angular frequency
w = 2 * %pi * f;
// Calculate impedance and admittance
Z = R + %i * w * L;
Y = G + %i * w * C;
// Characteristic impedance
```

```
Zo = sqrt(Z / Y);

C1 = round(real(Zo));

D1 = round(imag(Zo));

printf("Zo = %f + j(%f) ohms\n", C1, D1);

// Calculate propagation constant

P = sqrt(Z * Y);

// Attenuation constant

alpha = real(P);

alpha1 = round(alpha * 10000) / 10000;

printf("Attenuation constant = %f neper/km\n", alpha1);

// Phase constant

beta = imag(P);

beta1 = round(beta * 10000) / 10000;

printf("Phase constant = %f radians/km\n", beta1);
```

RESULTS

Test Case 1: The attached SCILAB output gives $Z_o = 14 - j2\ \Omega$, $\alpha = 0.3621$ neper/km and $\beta = 2.7769$ radians/km.

Test Case 2: The effect of resistance and inductance on Z_o, α and β was evaluated for the ranges specified in the manual.

Test Case 3: The effect of frequency and capacitance on Z_o, α and β was evaluated for the ranges specified in the manual.